

<i>Nom et Prénoms</i>			<i>Groupe</i>	<i>Note</i>
<i>Nom et Prénoms</i>				
<i>Date:</i>	<i>Horaire:</i>		<i>Lab. N°</i>	

Practical work: 2 Diode characteristics and rectification

I. Objectives

1. Study of diode characteristics.
2. Study of single-phase rectification.

II. Equipment used: The following equipment is used for this practical work:

- ri A stabilized power supply.
- ri Two digital multimeters.
- ri Connection cables and probes.
- ri Two resistors of **1k Ω** and **100 Ω** .
- ri One oscilloscope.
- ri Rectifier diodes.
- ri Two capacitors, **100 μ F** and **1000 μ F**.


III. Theoretical supplement:

III.1) Definition:

A diode is a non-linear, polarized (or non-symmetrical) dipole. A diode consists of a PN junction, in which current flows from the p-type material (anode) to the n-type material (cathode). The diode is the basic semiconductor component. Its operation is similar to that of a switch (which only allows current to flow in one direction) controlled by a voltage.



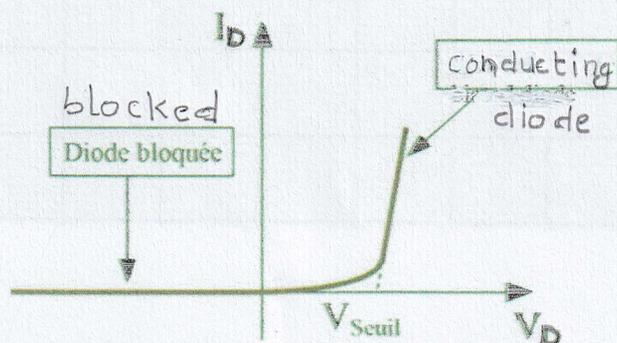The typical characteristic of a diode is shown in the following diagram:



$$r_d = \frac{\Delta V}{\Delta I} \quad (r_d: \text{dynamic resistance})$$


III.2) Applications:

One of the main applications of diodes is to convert an alternating signal, in which the direction of electron flow reverses every half-cycle, into a signal in which electrons flow in one direction only.

We have:


$$V_0(V_{moy}) = \frac{1}{T} \int_0^T K \{ t \} dt, \quad v_{2ff} = \int_{T_0}^1 U(t) dt, \quad f = \frac{1}{T}, \quad \omega = 2\pi f, \quad \phi = \omega t$$

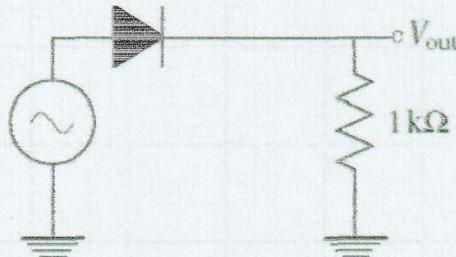III.2.1) Simple rectification irlternance.



$$V_0 = \frac{1}{2\pi} \int_0^{2\pi} \sin(\theta) d\theta, \quad \phi = \omega t$$

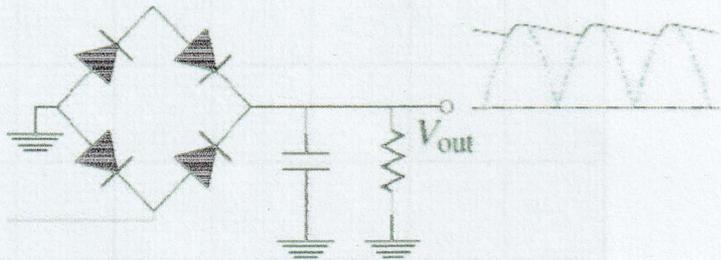III.2.2) Full-wave rectification and filtering:




-Le taux dRipple.- $\frac{\Delta V}{V_m} = \frac{1}{2RCf}$, $V_0 = V_m - \frac{\Delta V}{2}$, ($V_m = V_{max}$)

IV) Experimental study

1. Diode characteristics:

- Assemble the following diagram:

Complete the following table:

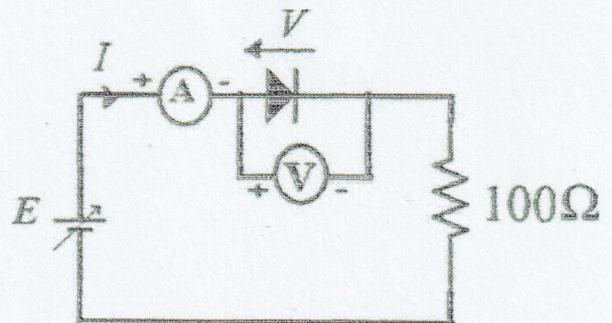

V(volts)	0	0.55	0.60	0.65	0.67	0.69	0.71	0.73	0.75	0.77
I(mA)										


2. Single-phase rectification

→ assembly of the following figure:

- Supply voltage: $V_e(t) = V_{e,m} \sin(314t)$,

→ Observe the AC supply voltage $V_e(t)$ on the oscilloscope then the voltage $V_R(t)$.

Record the following values.

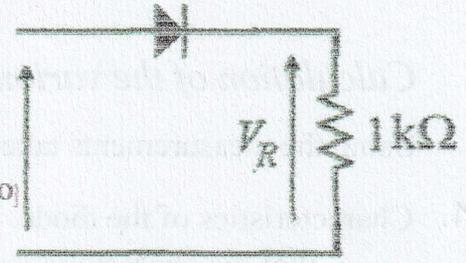

- La valeur maximale de $V_e(t)$: $V_{e,m} =$

- The period of $V_e(t)$: $T_e =$

- The maximum value of $V_R(t)$: $V_m =$

- The period of $V_R(t)$: $T =$

→ Reproduce the observed curves qualitatively (V_e and V_R) on graph paper.

→ Using the digital multimeter, measure

- The average value of $V_e(t)$ (DC mode) $V_{e,moy} =$

= The effective value of $V_e(t)$ (AC mode) $V_{e,eff} =$

The average value $V_R(t)$ (DC mode) $V_a =$

V. Calculation of the various parameters of the setup in the previous steps.

Using the measurements taken and the values recorded

1. Characteristics of the diode.

- Plot the characteristics of the diode on graph paper: $I = f(V)$.
- From this characteristic, deduce :

the threshold voltage of the diode and $V_d =$
 the dynamic resistance $r_d =$

2.. single-phase rectification

→ Calculate :

- The effective value, average value, and frequency of $V_e(t)$.

$$V_{eff} = \quad V_{e-moy} = \quad f_e =$$

- Calculate the effective value, average value, and frequency of U_q iŷ.



$$V_{eff} = \quad V_0 = \quad f =$$

- Compare these calculated values with those measured with the multimeter and with the given frequency (of $V_e(t)$).
- Compare the calculated values of U_q with those measured with the multimeter.


VI. Conclusion

Draw an appropriate conclusion regarding this TP.

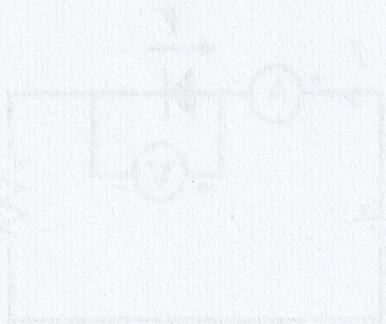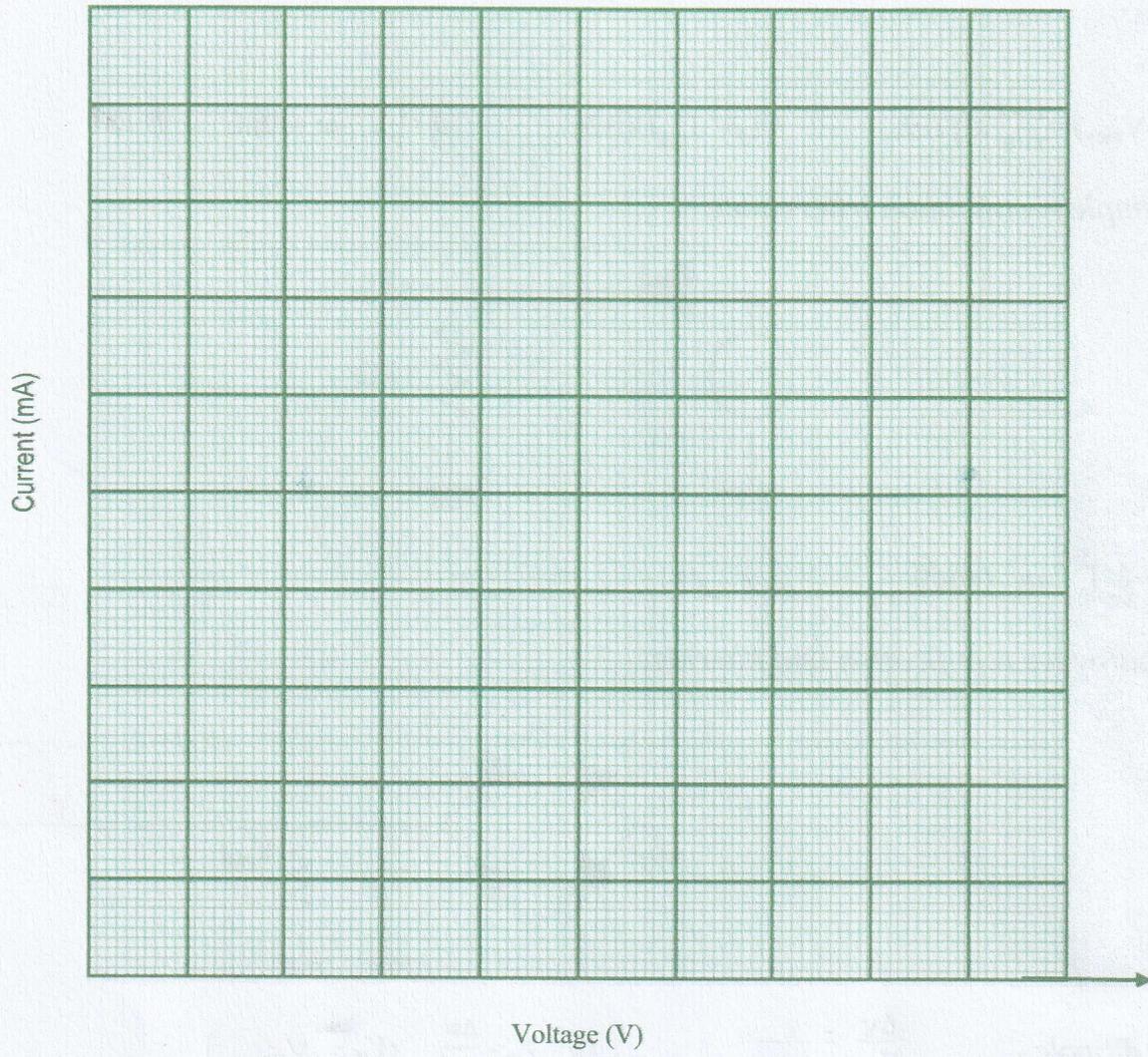
(1): Plot of the characteristic of iodine: $I=f(V)$.



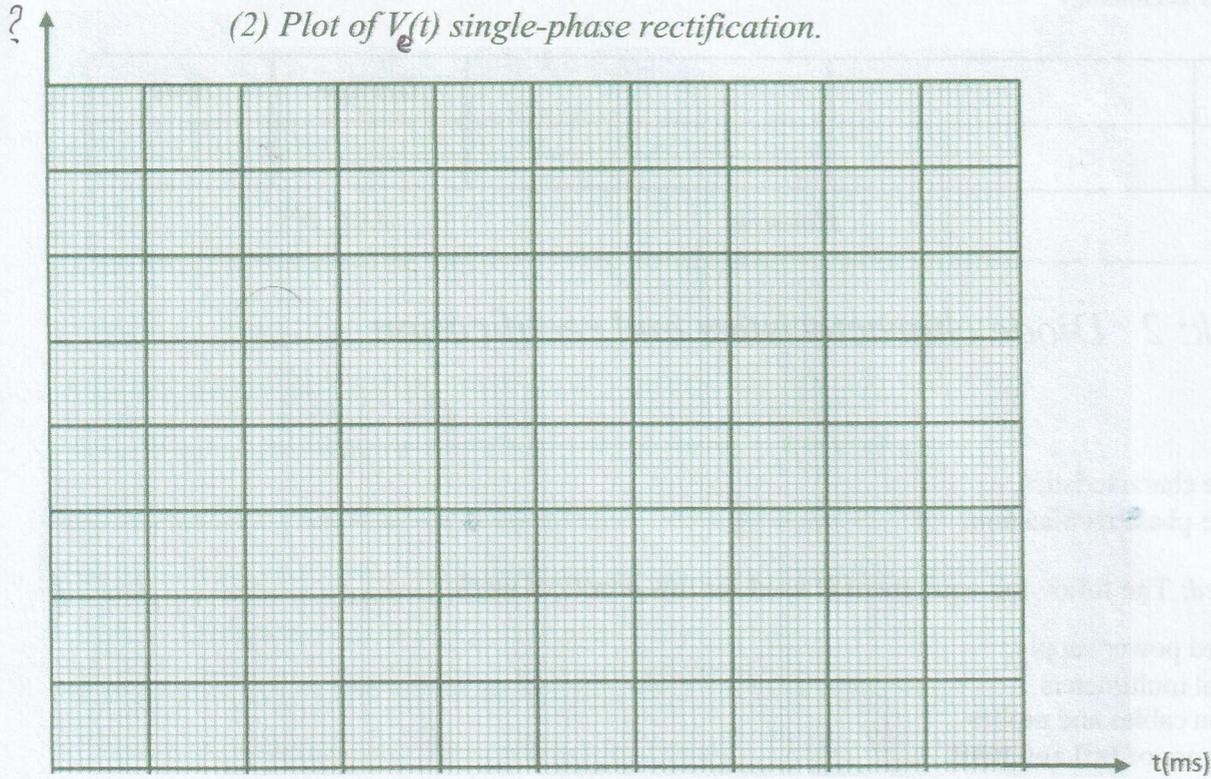(2) Plot of $V_{\theta}(t)$ single-phase rectification.



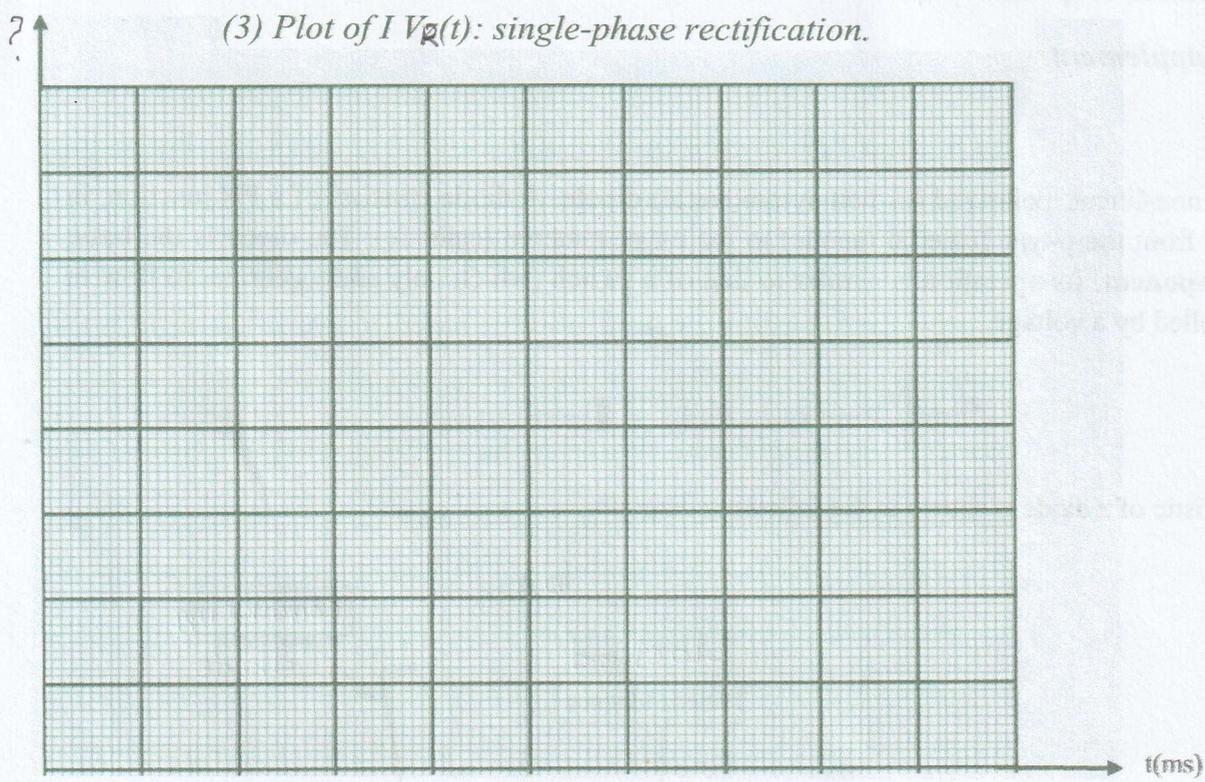(3) Plot of $I V_{\theta}(t)$: single-phase rectification.



VI) Comparison between theoretical and practical results

VII) Conclusion: draw an appropriate conclusion regarding this practical assignment.
