

<i>Nom et Prénoms</i>			<i>Groupe</i>	<i>Note</i>
<i>Nom et Prénoms</i>				
<i>Date:</i> <i>Horaire:</i> <i>Lab. N°</i>				

TP :3 Double alternating rectification and filtering

I. Objectifs:

1. Study of double-alternating recovery.
2. Study of capacitive filtering.


II. Equipment used : The following equipment is required for this practical assignment: :

- A stabilized power supply.
- Two digital multimeters.
- Connection cables and probes.
- Resistors **1kΩ** .
- An oscilloscope.
- Four rectifier diodes.
- Two capacitors of 100μF et 1000μF.

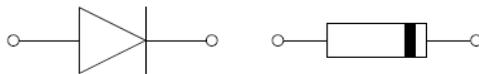
III. Complément théorique :

III.1) Définition :

A diode is a **nonlinear, polarized (or asymmetrical) dipole**. A diode consists of a PN junction, in which current flows from the p-type material (anode) to the n-type material (cathode). The diode is the basic **semiconductor component**. Its operation is similar to that of a switch (which only allows current to flow in one direction) controlled by voltage.



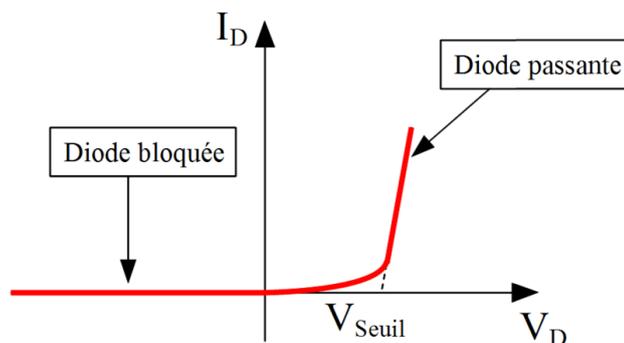La caractéristique typique d'une diode a l'allure représentée sur le schéma suivant :



$$r_d = \frac{\Delta V}{\Delta I} \quad (r_d: \text{dynamic resistance})$$


III.2) Applications:

One of the main applications of diodes is to transform an alternating signal, in which the direction of electron flow reverses every half-cycle, into a signal in which electrons flow in one direction only.

Given:


$$V_0(V_{\text{moy}}) = \frac{1}{T} \int_0^T V(t) dt, \quad V_{\text{eff}}^2 = \frac{1}{T} \int_0^T V^2(t) dt, \quad f = \frac{1}{T}, \quad \omega = 2\pi f, \quad \theta = \omega t$$

III.2.1) Redressement simple alternance:

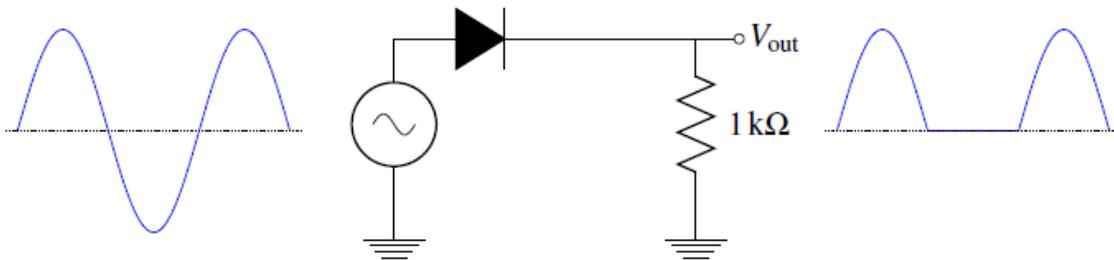

$$- V_0 = \frac{1}{2\pi} \int_0^{2\pi} \sin(\theta) d\theta$$

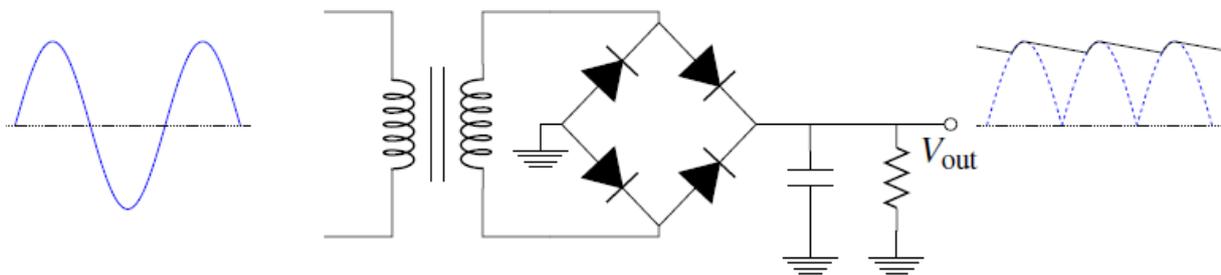III.2.2) Redressement double alternance et filtrage:




-Le taux d'ondulation: $\frac{\Delta V}{V_m} \approx \frac{1}{2RCf}$, $V_0 = V_m - \frac{\Delta v}{2}$ ($V_m = V_{\text{max}}$)

IV) Experimental Study

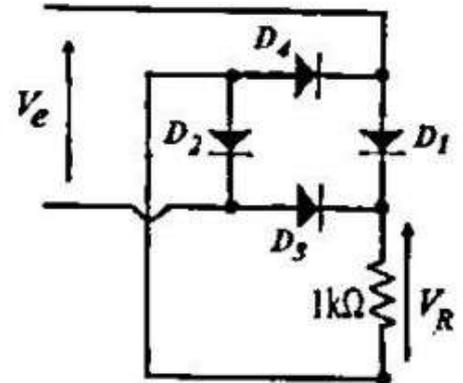1. Full-Wave Rectification

- Set up the circuit shown in the following figure:
- Observe the voltage $V_R(t)$ on the oscilloscope. Record the following values:

- The maximum value of $V_a(t)$: $V =$
- The period of $V_e(t)$: $T =$



- Qualitatively reproduce the observed $V_a(t)$ curve on graph paper.
- Using a digital multimeter, measure:

- The average value of $V_a(t)$ (DC mode) $V_0 =$


2. Capacitive Filtering

- Set up the circuit shown in the following figure:

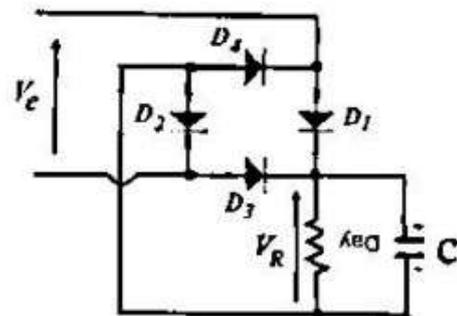4.1. For $C = 100 \mu F$

- Observe the voltage $V_R(t)$ on the oscilloscope. Record the following values:

- The maximum value of $V_R(t)$: $V_m =$
- The period of $V_R(t)$: $T =$
- The ripple: $\Delta V =$



- Qualitatively reproduce the observed curve $V_a(t)$ on graph paper.
- Using the digital multimeter, measure:

- The average value of $V_R(t)$ (DC mode) $V_0 =$

4.2. For $C = 1000 \mu F$

- Observe the voltage $V_R(t)$ on the oscilloscope. Record the following values:

- The maximum value of $V_a(t)$: $V =$
- The period of $V_a(t)$: $T =$

- Ripple: $\Delta V =$

- Qualitatively reproduce the observed curve $V_a(t)$ on graph paper.
- Using the digital multimeter, measure:

The average value $V_R(t)$ (DC mode) $V_o =$

V. Calculation of the different parameters of the circuit from the previous steps.

- Using the measurements taken and the recorded values:

1. Full-wave rectification

➤ Calculate:

- The RMS value, average value, and frequency of $V_a(t)$.

- $V_{eff} =$ $V_o =$ $f =$

- Compare these calculated values with those measured with the multimeter and with the given frequency (of $V_e(t)$).

2. Capacitive filtering

➤ Calculate:

- The ripple factor and the average value of $V_a(t)$ for $C = 100\mu F$.

$\frac{r_v}{V_m} =$ $V_o =$

- The ripple rate and the average value of $V_a(t)$ for $C = 1000\mu F$


$\frac{\Delta V}{V} =$ $V_o =$

- Compare the calculated values of V with those measured with the multimeter.

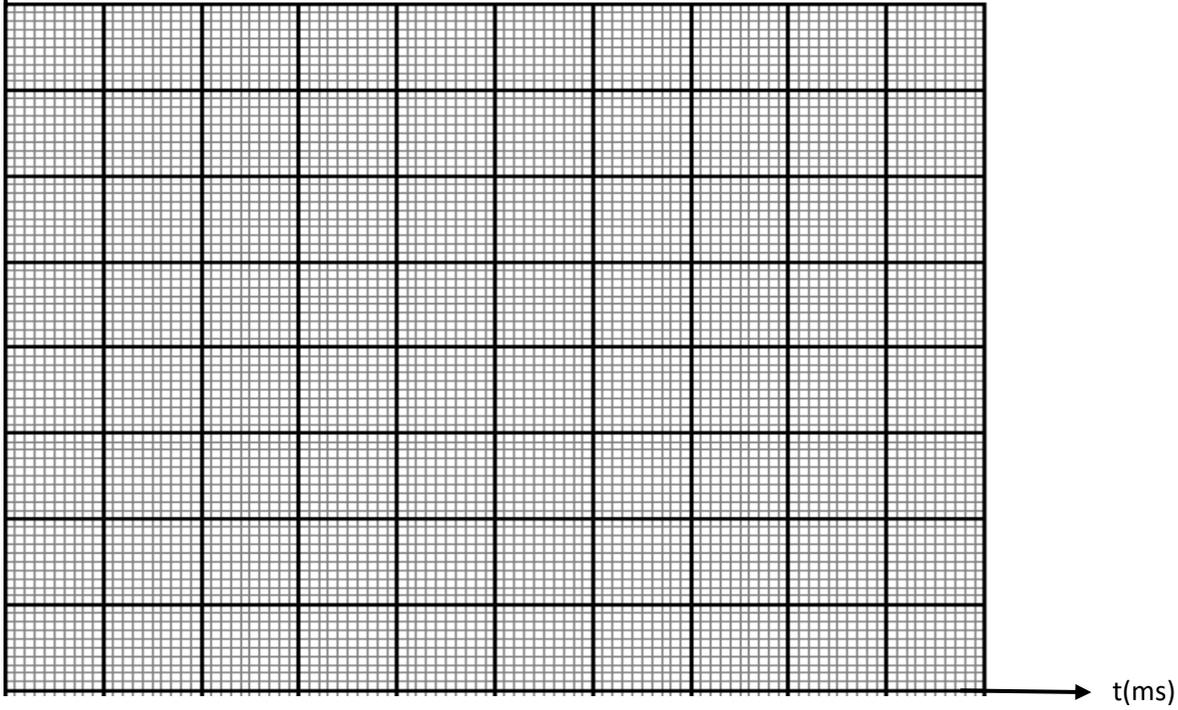
VI. Conclusion

- Draw a suitable conclusion regarding this lab


? ↑ (1) $V_R(t)$ tracing: *double alternating rectification.*



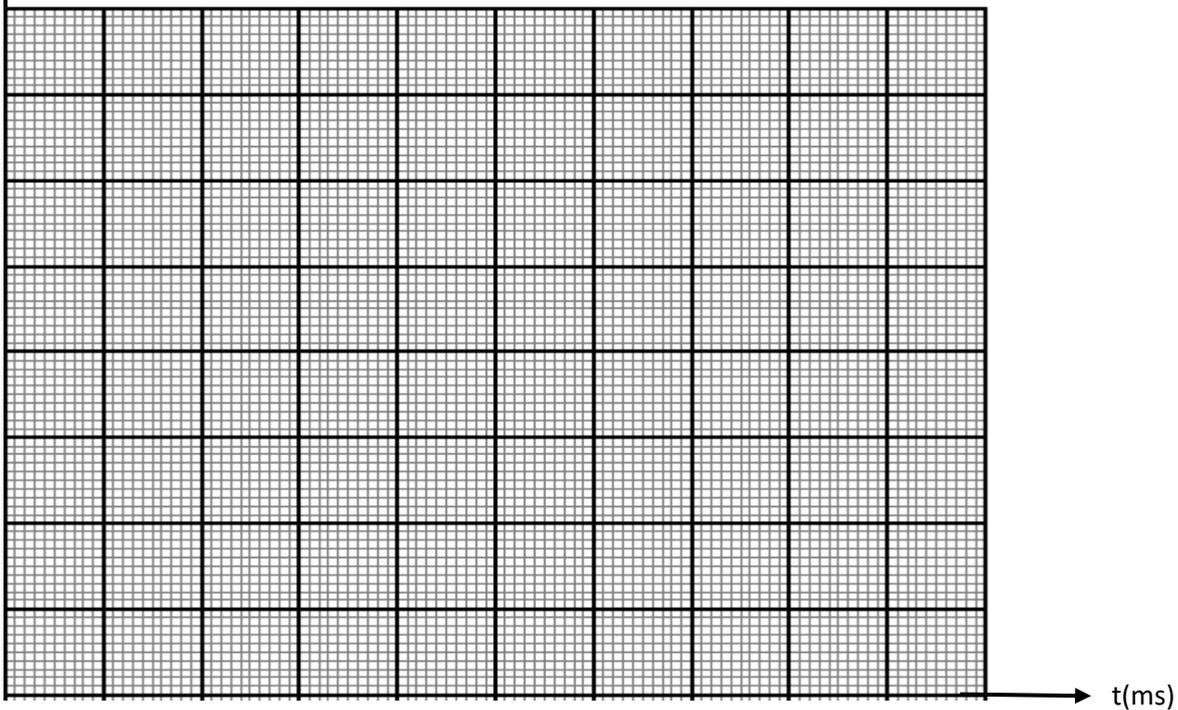? ↑ (2) $V_R(t)$ tracing: *capacitive filtering $C=100 \mu F$.*



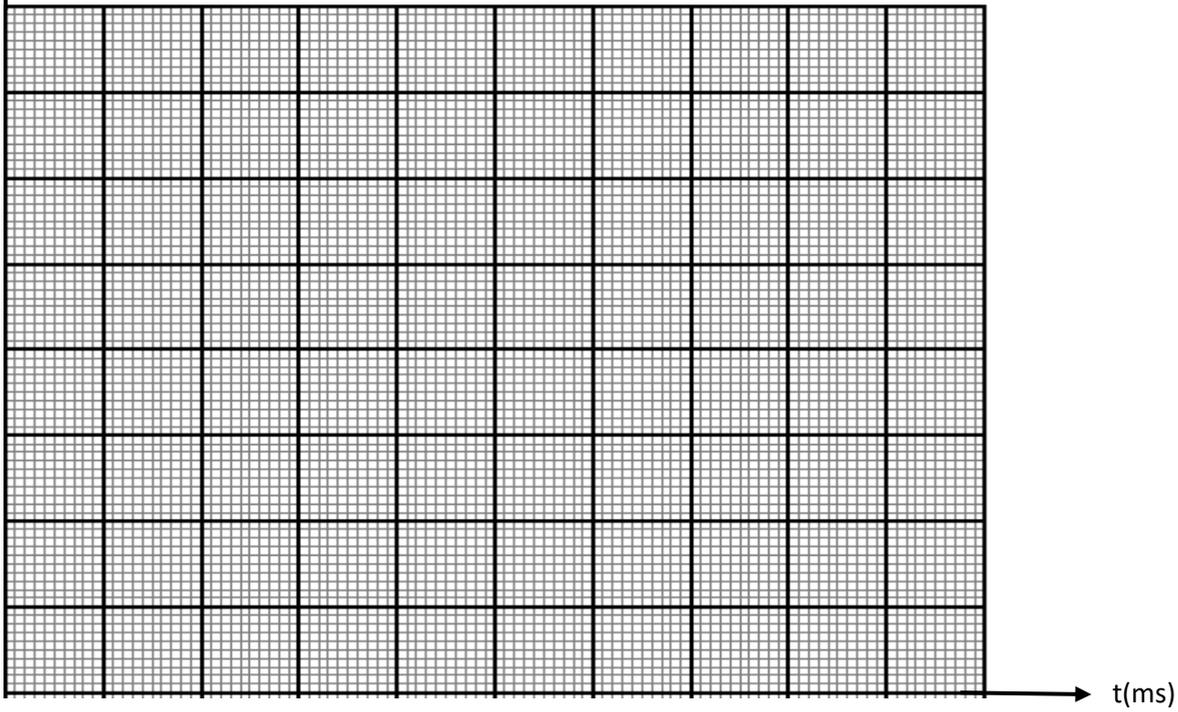↑ ? (3) $V_R(t)$ tracing: capacitive filtering $C=1000 \mu F$.



VI) Comparison between theoretical and practical results

VII) Conclusion: draw an appropriate conclusion about this practical assignment.
