

Bipolar Transistor

1. Objectives:

1. Plot the characteristics $I_C = f(V_{CE})$; $I_C = f(I_B)$ & $I_B = f(V_{BE})$ of the bipolar transistor;
2. Deduce the current amplifier function and calculate the current gain;
3. Understand the operation of the transistor.

11. Equipment Used: For this lab, the following equipment is used:

- Two regulated power supplies
- Three digital multimeters.
- Connecting cables.
- Two resistors of 10.2kΩ and 100.Ω.
- Two resistors of 43kΩ
- BC548B bipolar transistor.


III. Theoretical Study:

Must be done by the students in the group.

IV. Experimental Study

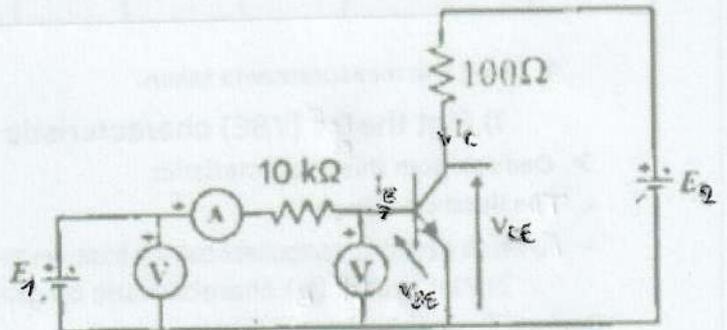1. Input characteristic $I_B = f(V_{BE})$


- Set up the circuit shown in the following figure:
- Set the voltage E_2 to 10 V
- Fill in the following table:



E_1 (V)	0	0.7	0.8	1	2	3	4	5	6	7	8	9
V_{BE} (mV)												
I_B (μA)												

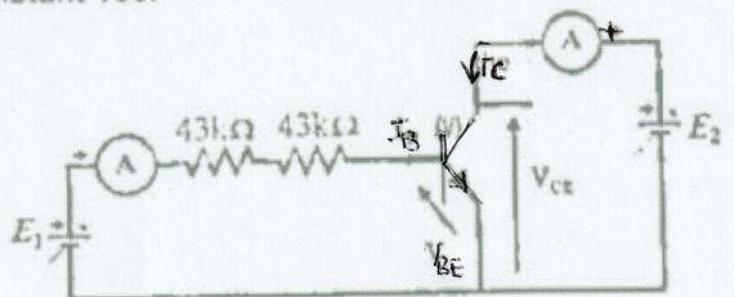2. Current transfer characteristic $I_C = f(I_B)$ at constant V_{CE} .

- Set up the circuit in the following figure:
- Set the voltage E_2 to 5 V
- By adjusting E_1 , vary I_B




- Fill in the following table:

I_B (μA)	0	10	20	30	40	50	60	70	80	90	100	110
I_C (mA)												

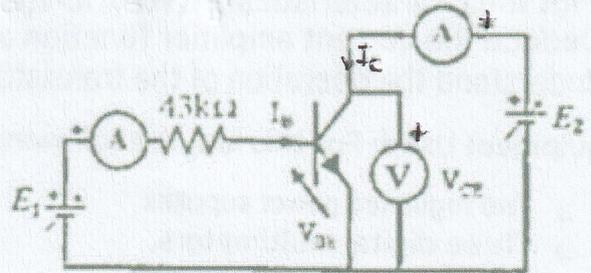3. Output Characteristic $I_C = f(V_{CE})$ at Constant I_B

- Set up the circuit in the following figure:



- Set the current to $200 \mu A$
- Vary E_2 and fill in the following table:

V_{CE} (V)	0	0.1	0.2	0.3	0.4	0.5	0.6	1	1.5	2	2.5	3
I_C (mA)												

V. Using the measurements taken.

1) Plot the $I_C = f(V_{BE})$ characteristic on graph paper

> Deduce from this characteristic:

- The threshold voltage
- To which electronic component can the base-emitter junction of the transistor be compared? Justify your answer.

2) Plot the $I_C = f(I_B)$ characteristic on graph paper at constant V_{CE}

Deduce from this characteristic:

The $\beta = I_C / I_B$. Compare this gain with that given by the constructor: $200 << 450$


3) Plot the $I_C = f(V_{CE})$ characteristic at constant voltage on graph paper.

> Deduce from this characteristic:

- The two operating regions of the transistor.

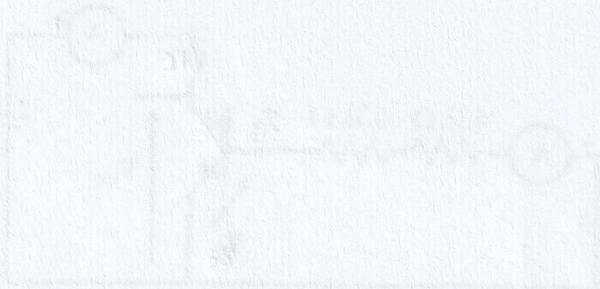VI. Conclusion


Draw a suitable conclusion regarding this lab



<i>Nom et Prénoms</i>			<i>Groupe</i>	<i>Note</i>
<i>Nom et Prénoms</i>				
<i>Date:</i> <i>Horaire:</i> <i>Lab. N°</i>				


1/

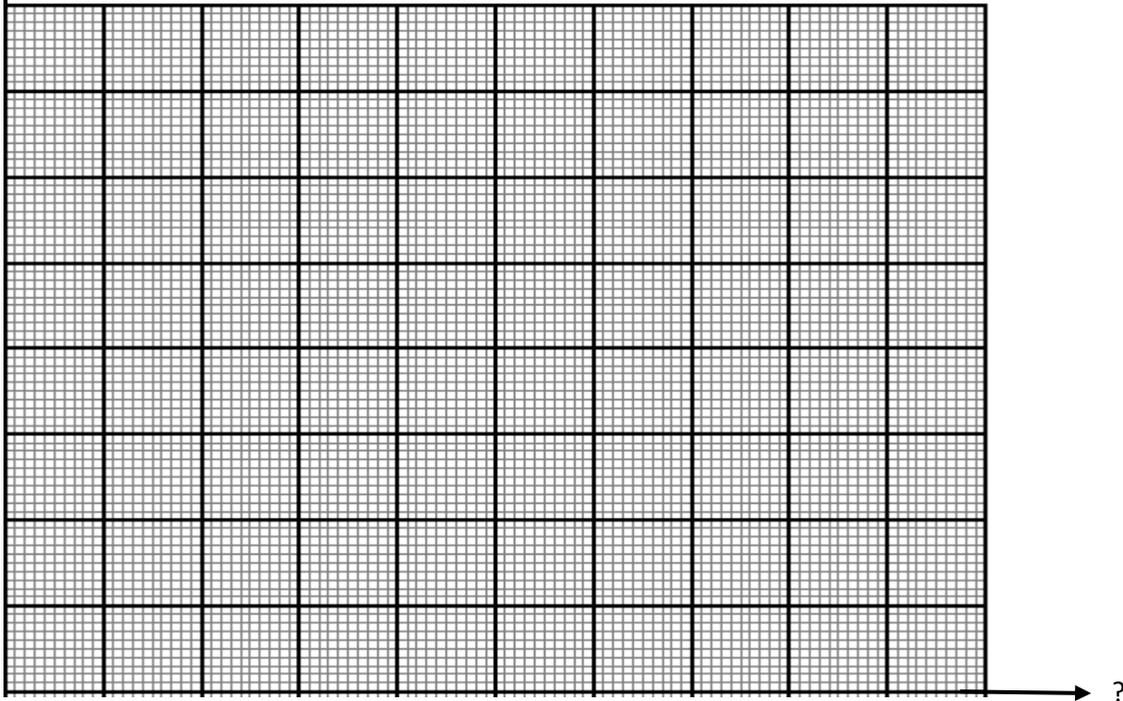? **Traceability of characteristics: $I_B = f(V_{BE})$**




2/

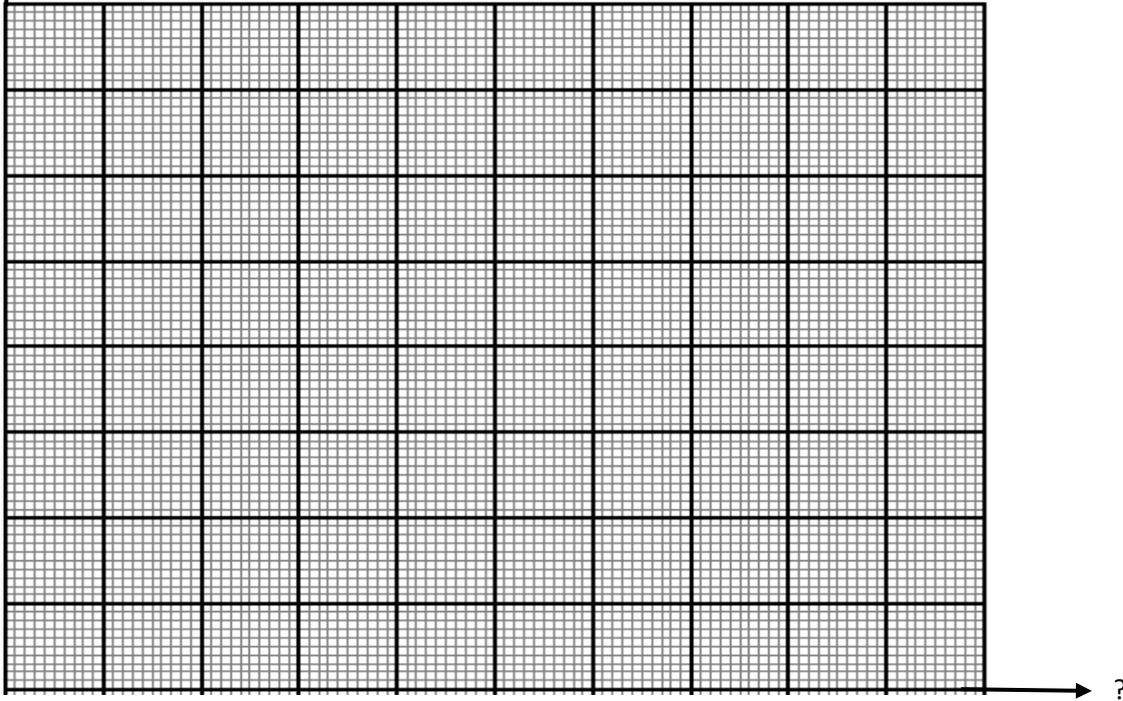? *Plotting the characteristic: $I_c = f(I_B)$*



3/

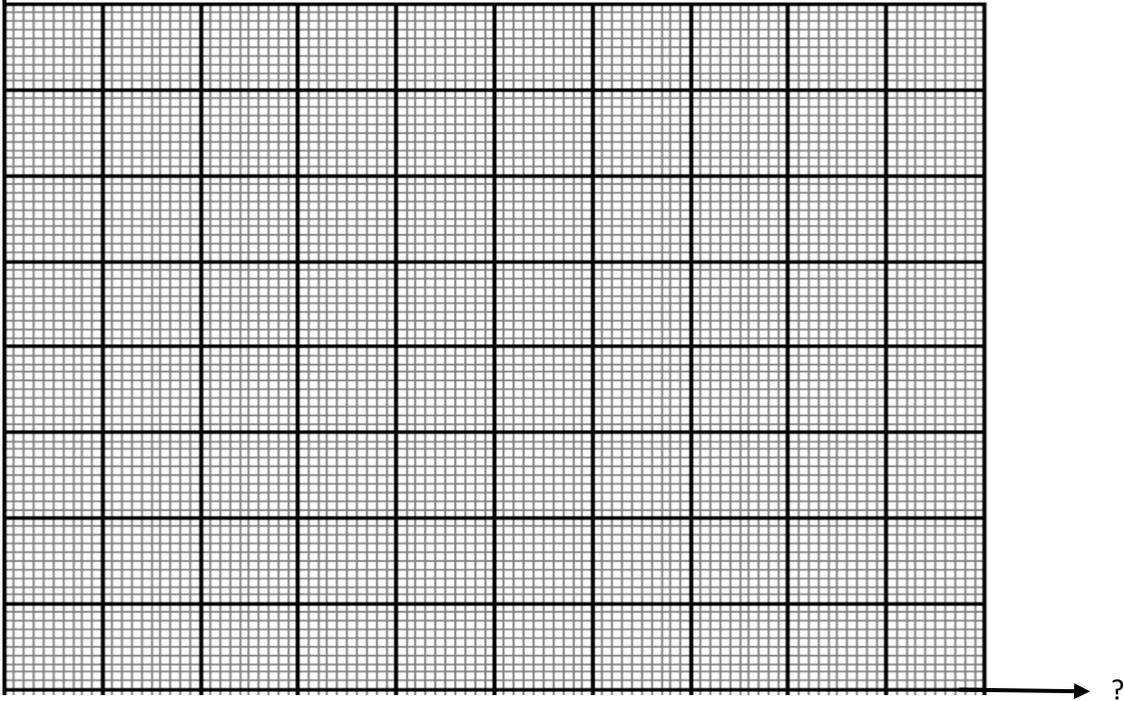? *Traceability of the characteristic: $I_C = f(V_{CE})$*



VII) Conclusion: draw an appropriate conclusion about this practical assignment.
