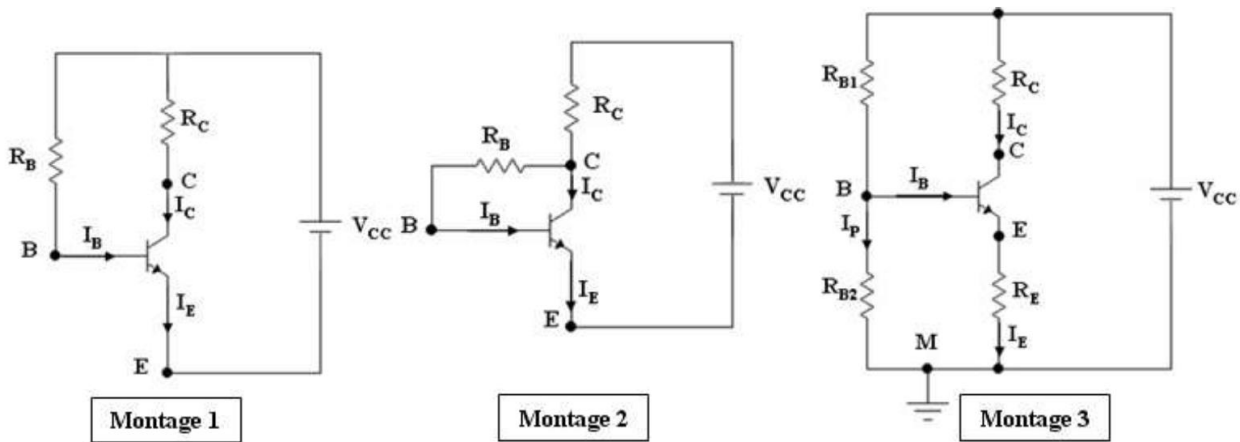


TD N° 2

Exercise 1: A silicon NPN transistor is used in the following three configurations:



1- Give the names of the polarization methods represented by these configurations.

2- Calculate the required biasing components.

For each configuration, the operating point should be as follows:

$$V_{CE_0} = 5 \text{ V}, I_{C_0} = 1 \text{ mA}, V_{CC} = 10 \text{ V}, \beta = 100, \text{ and } V_{BE_0} = 0.7 \text{ V}.$$

For configuration 3, take $I_p = 100 \mu\text{A}$ and $R_E = 1 \text{ k}\Omega$.

Exercise 2: Consider the circuit shown in the following figure:


1- Calculate the quiescent points (I_B , I_C , and V_{CE}).

2- Express and plot the lines: $I_C = f(V_{CE})$ and $I_B = f(V_{BE})$.

3- Represent the quiescent points on their respective lines.

Given: $\beta = 180$, $V_{BB} = 5 \text{ V}$, $V_{CC} = 10 \text{ V}$, $V_{BE} =$

0.6 V , $R_B = 10 \text{ k}\Omega$, and $R_C = R_E = 100 \Omega$.

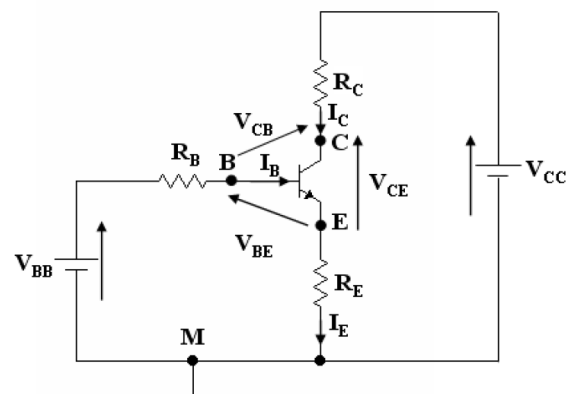

Exercise 3: Consider the following circuit with an NPN

transistor having a current gain $\beta = 200$ and a base-emitter voltage

$V_{BE} = 0.7 \text{ V}$.

1- Calculate the currents I_B , I_E , and I_C .

2- Calculate the voltages U_E and U_C .

3- Determine the collector-emitter voltage U_{CE} .

4- Calculate the collector-base voltage U_{CB} .

Given values: $U = 3.4 \text{ V}$, $R_1 = 4.7 \text{ k}\Omega$, $R_2 = 2.7 \text{ k}\Omega$, and $V_{CC} =$

10 V .

